

BE1M13VES

Manufacturing of Electrical Components

Michal Brejcha

CTU in Prague

Prague, 2017

Overview

- 1 Terms
- 2 Basic Circuit Components
- 3 Basic Circuits

TOPIC

1 Terms

2 Basic Circuit Components

3 Basic Circuits

Scattering vs Discrete

- Discrete:
- The description of the system is given by a specific count of discrete parts (components), that are connected via ideal conductors.
 - There are only slow changes of the signals. Therefore the time of signal propagation in the system is negligible. The signal level depends only on the time (time is only variable).

- Scattering:
- The description of the system is given by scattering parameters.
 - There are fast changes of the signals. The signal propagation depends on time and also on position coordinates in the system.

Linear vs Nonlinear

Linear ■ The system dependency is described only by linear equations.

■ The superposition can be used.

Nonlinear ■ The system dependency is described by nonlinear equations.

■ They create other harmonic frequencies for harmonic signals. The superposition cannot be used.

Passive component vs Active component

- Passive** ■ It only dissipates or cumulates the electric energy in electrostatic or magnetic field: resistors, capacitors, inductors, ...
- Active** ■ It contains sources of energy: transistors, amplifiers, sources, ...






TOPIC

1 Terms




2 Basic Circuit Components

3 Basic Circuits

Most Common Circuit Components

Component	Symbol	Units	Type
Voltage source		Volts (V)	Active
Current source		Amps (A)	Active
Resistor		Ohms (Ω)	Passive
Kapacitor		Farads (F)	Passive
Inductor		Henry (H)	Passive

Passive Components

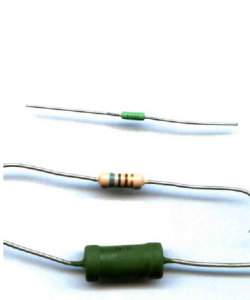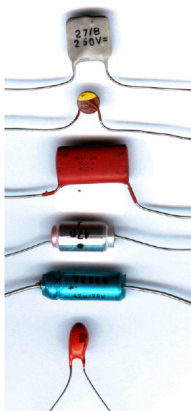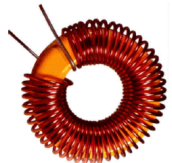*a)**b)**c)*

a) Resistors, *b)* Capacitors, *c)* Inductors

Resistor

Basic parameters: electric resistivity (R),
dissipated power (P_{max})


Energy: electrical energy \Rightarrow heat
 $P = u \cdot i = u^2 / R = R \cdot i^2$

u ... instantaneous voltage
 i ... instantaneous current

Connection:

$R_{total} = \sum R$
serial



$1/R_{total} = \sum 1/R$
shunt

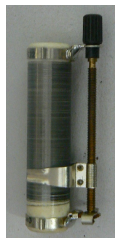

Ideal Resistor in a Circuit

Ohms law:

$$u(t) = R \cdot i(t)$$

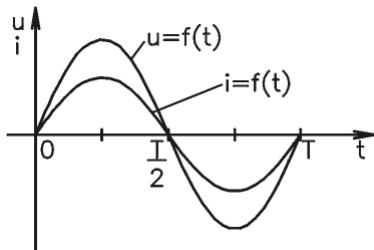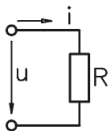

Phasor:

$$\text{Im} \left\{ \hat{U} \cdot e^{j\omega t} \right\} = R \cdot \text{Im} \left\{ \hat{I} \cdot e^{j\omega t} \right\}$$

$$\hat{U} = R \cdot \hat{I} \dots \hat{U}, \hat{I} \text{ no difference in phase}$$

Capacitor

Basic parameters: capacitance (C),
nominal voltage (U)

Energy: electrical energy \Rightarrow
electrical field
 $q = C \cdot u$
 $E = C \cdot u^2 / 2 = q \cdot u / 2$





u ... instantaneous voltage
 q ... instantaneous charge

Connection:

$1/C_{total} = \sum 1/C$
serial

$C_{total} = \sum C$
shunt

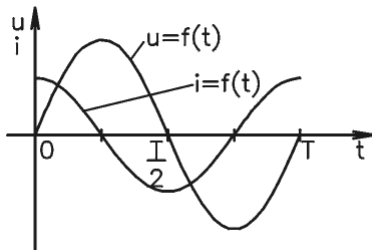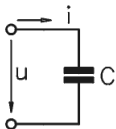Current equation: $i(t) = C \cdot \frac{\partial u(t)}{\partial t}$



Phasor:


$$Im \left\{ \hat{I} \cdot e^{j\omega t} \right\} = C \cdot \frac{\partial Im \{ \hat{U} \cdot e^{j\omega t} \}}{\partial t}$$

$$\hat{I} = j\omega C \cdot \hat{I} \dots \hat{U} \text{ is delayed for } 90^\circ \text{ after } \hat{I}$$

Inductor

Basic parameters: inductance (L),
nominal current (I)

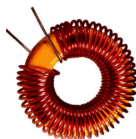Energy: electrical energy \Rightarrow
magnetic field
 $\phi = L \cdot i$
 $E = L \cdot i^2 / 2 = \phi \cdot i / 2$



i ... instantaneous current
 ϕ ... instantaneous flux



Connection:

$L_{total} = \sum L$
serial

$1/L_{total} = \sum 1/L$
shunt

Ideal Inductor in a Circuit

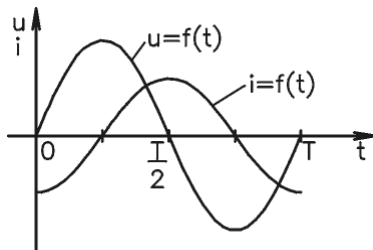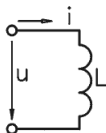Induced voltage: $u(t) = L \cdot \frac{\partial i(t)}{\partial t}$



Phasor:

$$\text{Im} \left\{ \hat{U} \cdot e^{j\omega t} \right\} = L \cdot \frac{\partial \text{Im} \left\{ \hat{I} \cdot e^{j\omega t} \right\}}{\partial t}$$

$$\hat{U} = j\omega L \cdot \hat{I} \dots \hat{U} \text{ is ahead of } \hat{I} \text{ for } 90^\circ$$

TOPIC

1 Terms

2 Basic Circuit Components

3 Basic Circuits