

# BE1M13VES

## Manufacturing of Electrical Components

Michal Brejcha

CTU in Prague

Prague, 2017

# Overview


- 1 Frequency dependency of resistors
- 2 Frequency dependency of capacitors
- 3 Frequency dependency of inductors
- 4 Notes

# TOPIC

- 1 Frequency dependency of resistors
- 2 Frequency dependency of capacitors
- 3 Frequency dependency of inductors
- 4 Notes
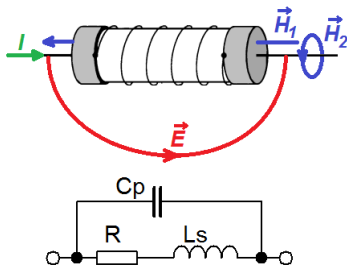
# Equivalent Circuit

For AC circuits the parasitic serial inductance and parallel capacity must be taken into account. The frequency dependence of the resistors is caused especially by its construction.




- $H_1, H_2...$  magnetic field from resistive track and leads.
- $E...$  electric field (capacitance) between opposite sides of package and leads.

# Technology Overview

- Parasitic capacitance is dominant for higher values of resistance ( $> \text{k}\Omega$ ).
- Parasitic inductance is dominant only for small values of resistance ( $< 100\Omega$ ) and frequencies smaller than resonant frequency.
- Larger packages have larger parasitic inductance
  - power resistors (resistive wire) - worst
  - small smd thin film resistors - best



# Impedance Plot Example

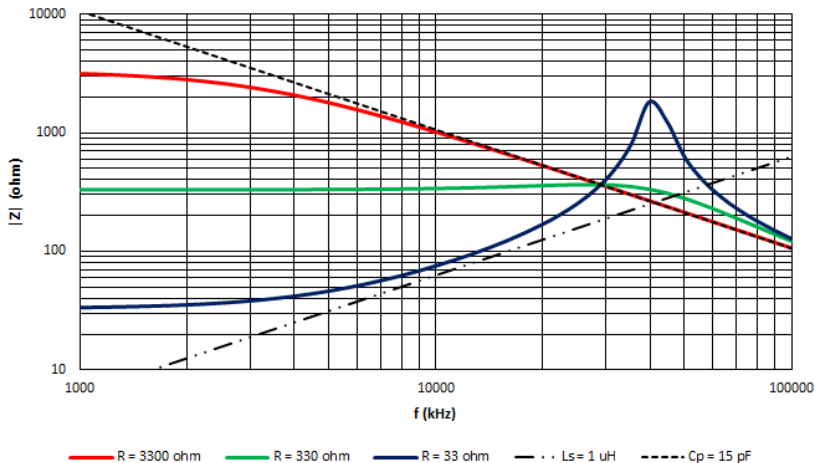

# Equivalent Circuit Analysis

Impedance:

$$\hat{Z} = \frac{R - \frac{j}{\omega C_p} \cdot \left( \omega^2 L_s C_p \cdot (\omega^2 L_s C_p - 1) + (\omega C_p R)^2 \right)}{(1 - \omega^2 L_s C_p)^2 + (\omega C_p R)^2}$$

Low frequencies ( $\omega \rightarrow 0$ ): **resistivity**

$$\hat{Z} \approx R$$

High frequencies ( $\omega \gg \omega_{RES}$ ): **parasitic capacitance effect**

$$\hat{Z} \approx \frac{1}{j\omega C_p}$$

# Equivalent Circuit Analysis - Resonance

Resonance frequency:

$$\omega_{RES} = \sqrt{\frac{1}{L_s C_p} - \left(\frac{R}{L_s}\right)^2}$$

Impedance at  $\omega_{RES}$


$$\hat{Z}_{RES} = \frac{Z_0^2}{R}$$

Where  $Z_0$  has the same definition as wave impedance:

$$Z_0 = \sqrt{\frac{L_s}{C_p}}$$



# Analysis Example

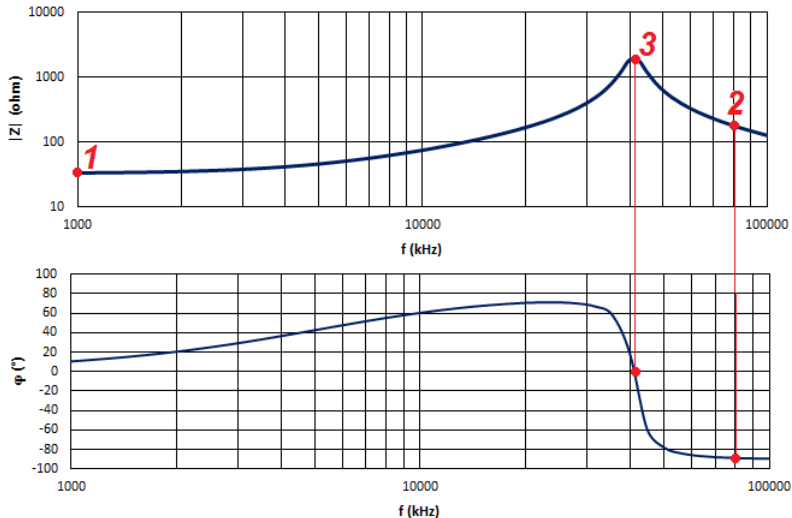

# Analysis Example

**1** Resistance:

$$R = 33\Omega$$

**2** Capacitance (**15 pF**):

$$C_p \approx \frac{1}{\omega \cdot |Z|} = \frac{1}{503 \cdot 10^6 \cdot 180} = 11pF$$



**3** Inductance (**1  $\mu$ H**):

$$L \approx Z_{RES} \cdot R \cdot C_p = 1900 \cdot 33 \cdot 15 \cdot 10^{-12} = 940nH$$

# TOPIC

- 1 Frequency dependency of resistors
- 2 Frequency dependency of capacitors**
- 3 Frequency dependency of inductors
- 4 Notes

# Equivalent Circuit

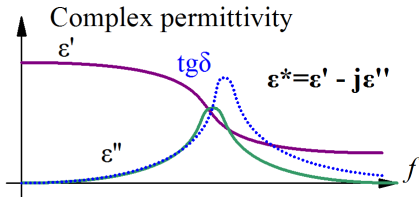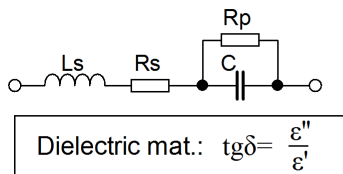

Frequency dependence due to package properties:



- Parasitic inductance of the leads and electrodes  $L_s$ .
- Parasitic resistance of the leads  $R_s$ .

Frequency dependence due to material properties (complex permittivity):


- Change in dielectric power dissipation  $R_p$  ( $\epsilon''$ ) - dissip. factor ( $D$ ).
- Change in capacity  $C$  ( $\epsilon'$ ).
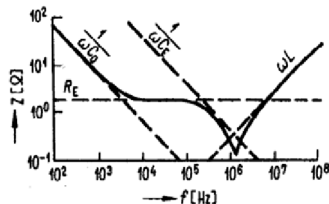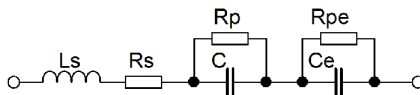
# Technology Overview

- Capacitors with higher capacitance have lower resonant frequency.
- Foil capacitors have larger parasitic inductance  $L_s$ .
- Electrolytic capacitors have higher serial parasitic resistance  $R_s$  due to electrolyte presence.
- Equivalent scheme of electrolytic capacitor:



# Impedance Plot Example

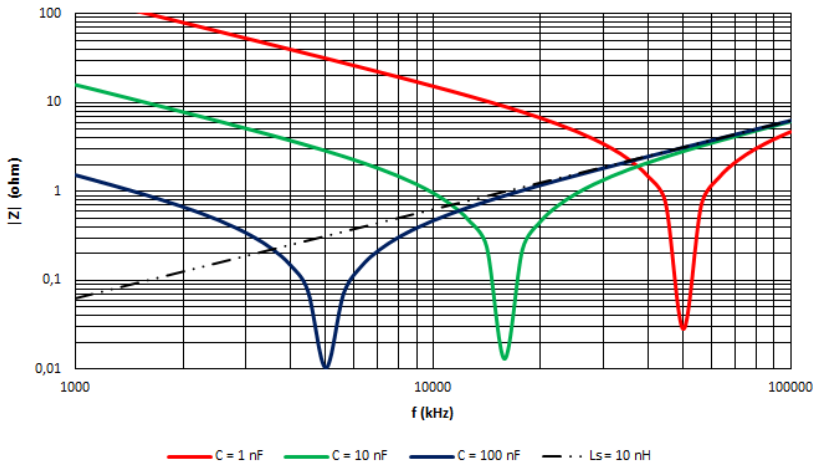

# Equivalent Circuit Analysis

Impedance:

$$\hat{Z} = R_s + \frac{R_p}{(1 + (\omega CR_p)^2)} + j \left( \omega L_s - \frac{1}{\omega C} \cdot \frac{(\omega CR_p)^2}{(1 + (\omega CR_p)^2)} \right)$$

Low frequencies ( $\omega \ll \omega_{RES}$ ): **capacitance**

$$\hat{Z} \approx \frac{1}{j\omega C}$$

High frequencies ( $\omega \gg \omega_{RES}$ ): **parasitic inductance**

$$\hat{Z} \approx j\omega L_s$$

# Equivalent Circuit Analysis - Resonance

Resonance frequency:

$$\omega_{RES} = \sqrt{\frac{1}{L_s C} - \left(\frac{1}{R_p C p}\right)^2} \approx \sqrt{\frac{1}{L_s C}}$$


Impedance at  $\omega_{RES}$

$$\hat{Z}_{RES} = R_s + \frac{Z_0^2}{R_p} \approx R_s$$

- The approximation is made for capacitors with high resistance  $R_p$  and value of capacitance  $C > 1 \text{ nF}$
- The higher resistance at the resonance is caused by the factor  $\frac{Z_0^2}{R_p}$  or by **skin-effect**.
- The parasitic resistances can change due to frequency dependence of complex permittivity.



# Analysis Example

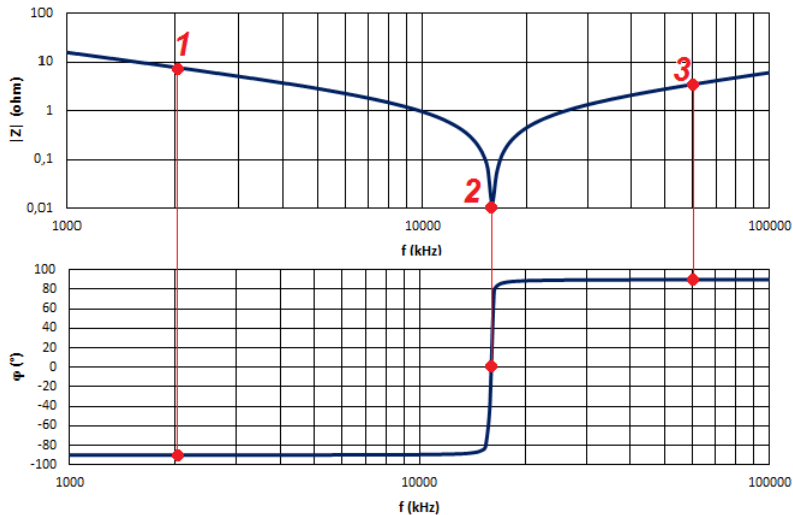

# Analysis Example

1 Capacitance (**10 nF**):

$$C \approx \frac{1}{\omega \cdot |Z|} = \frac{1}{12.6 \cdot 10^6 \cdot 7.85} = 10.1 nF$$

2 Serial resistance **0.01 Ω**):

$$R_s \approx Z_{RES} = 0.01 \Omega$$



3 Inductance (**10 nH**):

$$L \approx \frac{|Z|}{\omega} = \frac{3.65}{376 \cdot 10^6} = 9.7 nH$$

# TOPIC

- 1 Frequency dependency of resistors
- 2 Frequency dependency of capacitors
- 3 Frequency dependency of inductors**
- 4 Notes

# Equivalent Circuit

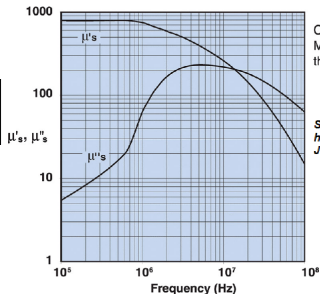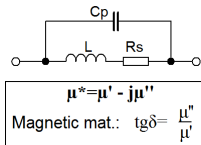


Complex Permeability vs. Frequency  
 Measured on a 17/10/6mm toroid using  
 the HP 4284A and the HP 4291A.

Source:  
[http://www.nutsvolts.com/magazine/article/July2015\\_HamWorkbench](http://www.nutsvolts.com/magazine/article/July2015_HamWorkbench)

- The same equivalent circuit as in case of resistors.
- The frequency dependence strongly affected by core material properties and skin-effect.
- Coils with high impedance have lower resonant frequencies.

# Impedance Plot Example

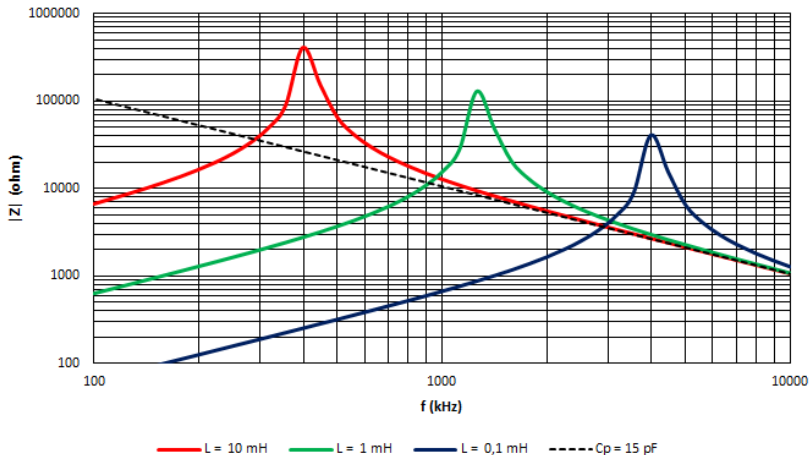

# Equivalent Circuit Analysis

Very low frequencies ( $\omega \rightarrow 0$ ): **parasitic resistivity**

$$\hat{Z} \approx R_s$$


Low frequencies ( $\omega \ll \omega_{RES}$ ): **inductance**

$$\hat{Z} \approx j\omega L$$

High frequencies ( $\omega \gg \omega_{RES}$ ): **parasitic capacitance effect**

$$\hat{Z} \approx \frac{1}{j\omega C_p}$$

# Analysis Example

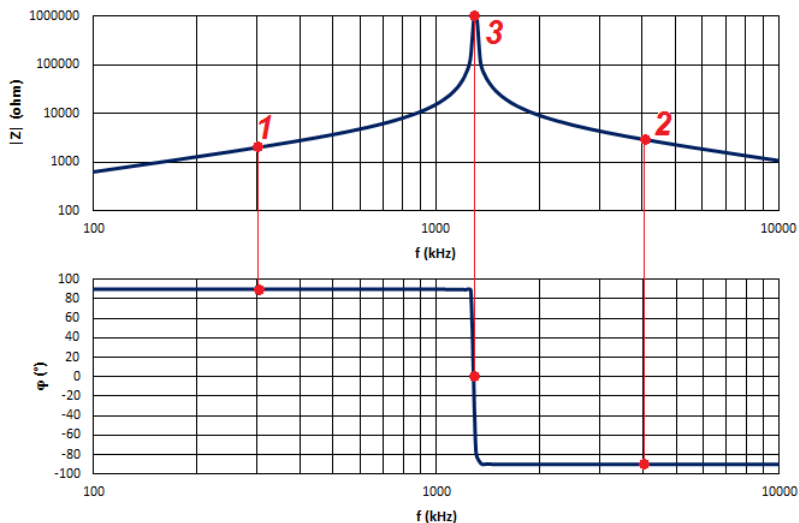

# Analysis Example

- 1 Inductance (**1 mH**):

$$L \approx \frac{|Z|}{\omega} = \frac{2050}{1885 \cdot 10^3} = 1.1 \text{ mH}$$

- 2 Parallel capacitance (**15 pF**):

$$C \approx \frac{1}{\omega \cdot |Z|} = \frac{1}{25.1 \cdot 10^6 \cdot 2970} = 13 \text{ pF}$$

- 3 Serial resistance **10 Ω**):

$$R_s \approx \frac{Z_0^2}{Z_{RES}} = \frac{10^{-3}}{1510^{-12} \cdot 10^6} = 6.67 \Omega$$

- **NO!** ... better to find out the serial resistance from DC measurement.



# TOPIC

- 1 Frequency dependency of resistors
- 2 Frequency dependency of capacitors
- 3 Frequency dependency of inductors
- 4 Notes**

# NOTES

- In case of impedance plot use logarithmic scale for both axis.
- In case of phase plot use logarithmic scale only for frequency.

■

$$\hat{Z} = R + jX$$

■

$$|Z| = \sqrt{R^2 + X^2}$$

■

$$\varphi = \operatorname{arctg} \frac{X}{R}$$

- resonance:  $X = 0$ ,  $\varphi = 0$ , parallel  $\Rightarrow$  high  $|Z|$ , serial  $\Rightarrow$  low  $|Z|$